



## LAB #75

### STEP 6



Source Voltage: 12.0 V

### STEP 10



Known Resistor Resistance:  $50 \times 10^{-1} \pm 1\% \Omega$



### STEP 13

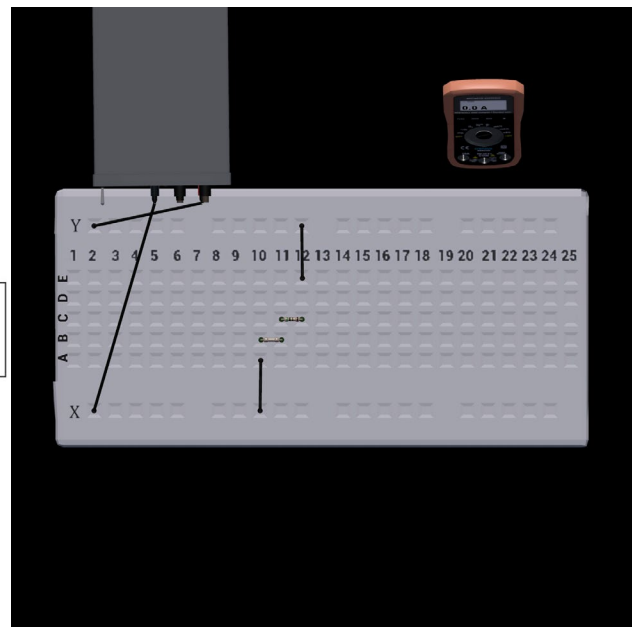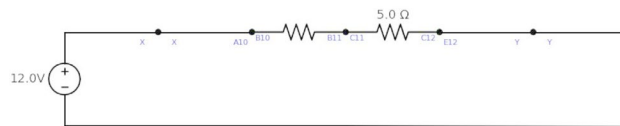



### **STEP 17**

Known Resistor Voltage: 4.0 V

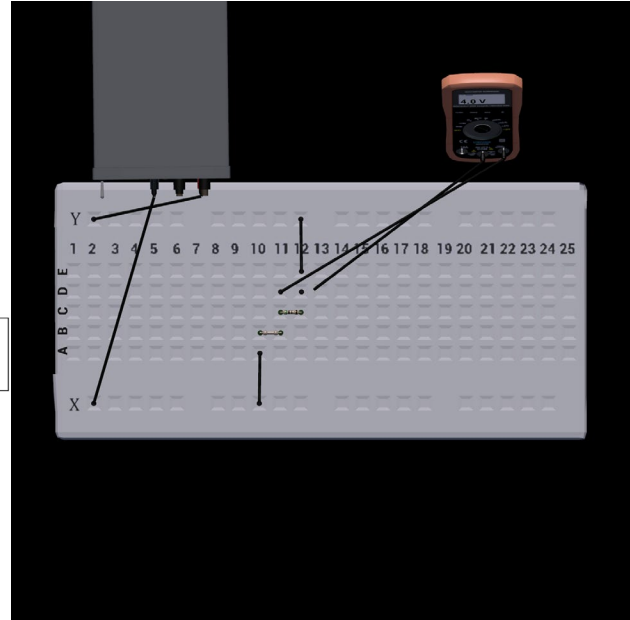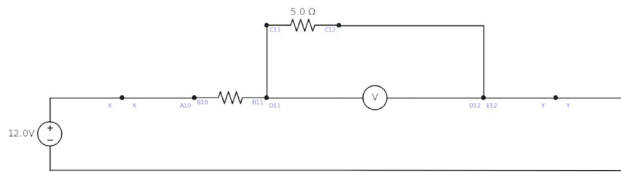

### **STEP 19**

Known Resistor Current:

By Ohm's law :  $V=RI \rightarrow I = 4.0 \text{ V} / 5 \Omega = 0.8 \text{ A}$

By Kirchhoff law, it's the current of the entire system.

### **STEP 20**

Kirchhoff Law :  $P = V_1 + V_2$

$V_2 = 12.0 \text{ V} - 4.0 \text{ V} = 8.0 \text{ V}$

By Ohm's law :  $V=RI \rightarrow R = 8.0 \text{ V} / 0.8 \text{ A} = 10.0 \Omega$