





LAB #076

STEP 1

Voltage at the source: 12 V



STEP 12

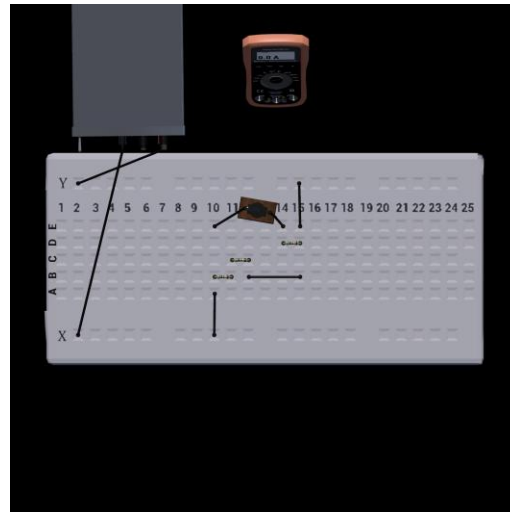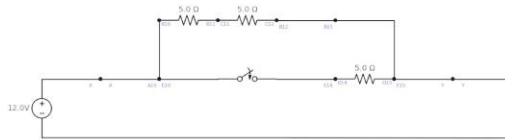

STEP 17


Current Bottom Branch: 2.4 A

STEP 18

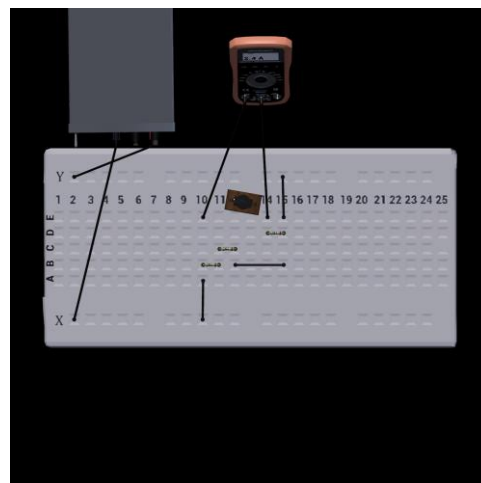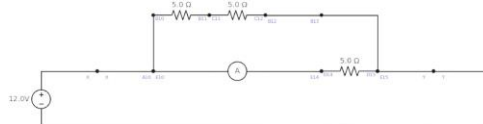



STEP 19

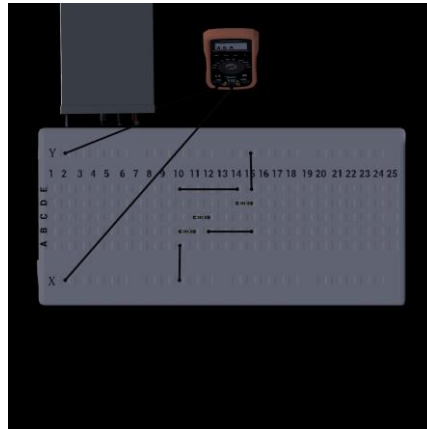



Current Source: 3.6 A

STEP 20

Kirchhoff's First Law : $I_s = I_1 + I_2 = \dots$

Current Top Branch = 1.2 A

STEP 21

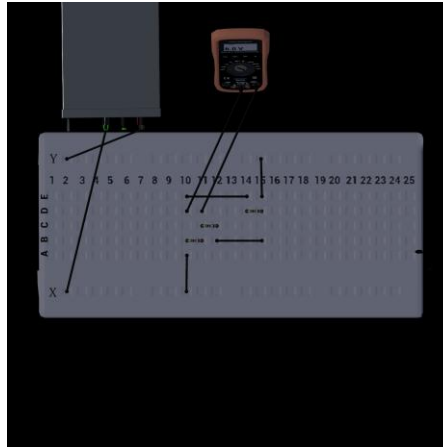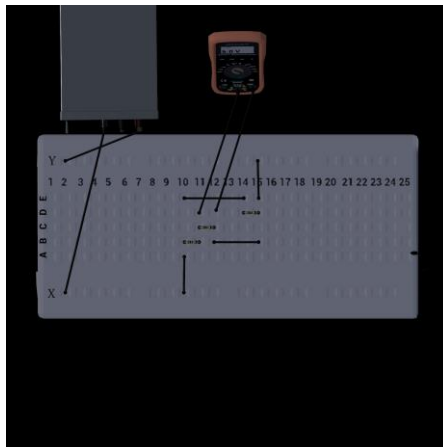

Voltage Resistor 1 = Voltage Resistor 2 = 6.0 V

STEP 22

Ohm's Law : $V = RI$

Resistance Resistor 1 = $6.0 \text{ V} / 1.2 \text{ A} = 5 \Omega$

Resistance Resistor 2 = $6.0 \text{ V} / 1.2 \text{ A} = 5 \Omega$